

$$(3) r_i = R_E \parallel \frac{r_{be}}{1+\beta} = 2.9k\Omega \parallel \frac{1.4k\Omega}{101} = 14\Omega$$


$$(4) r_o = R_C = 2.1k\Omega$$

$$(5) R_S = 50\Omega \text{ 时}$$


$$A_{us} = A_u \cdot \frac{r_i}{r_i + R_S} = 10.6$$

1.24


交流通路:

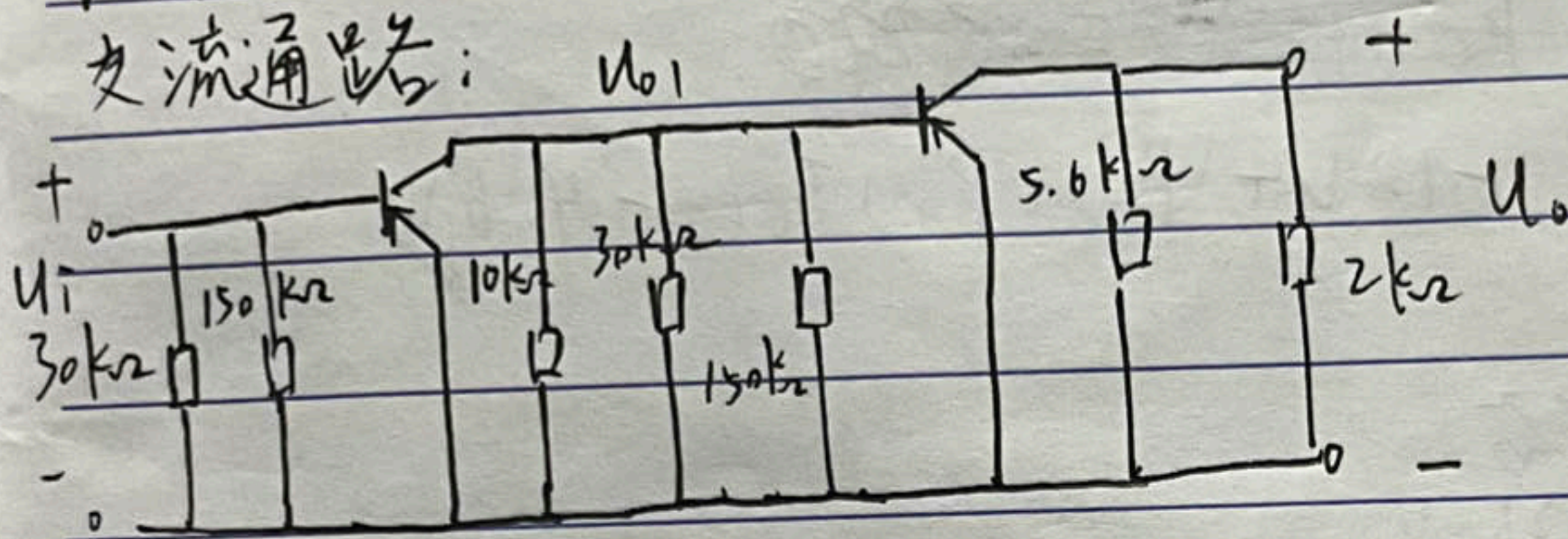

微变等效:

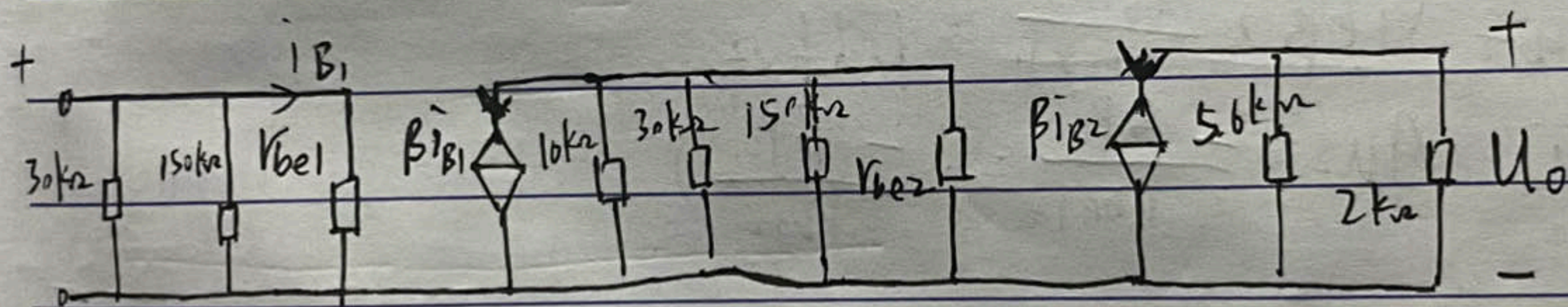

(1) 对第一级电路:

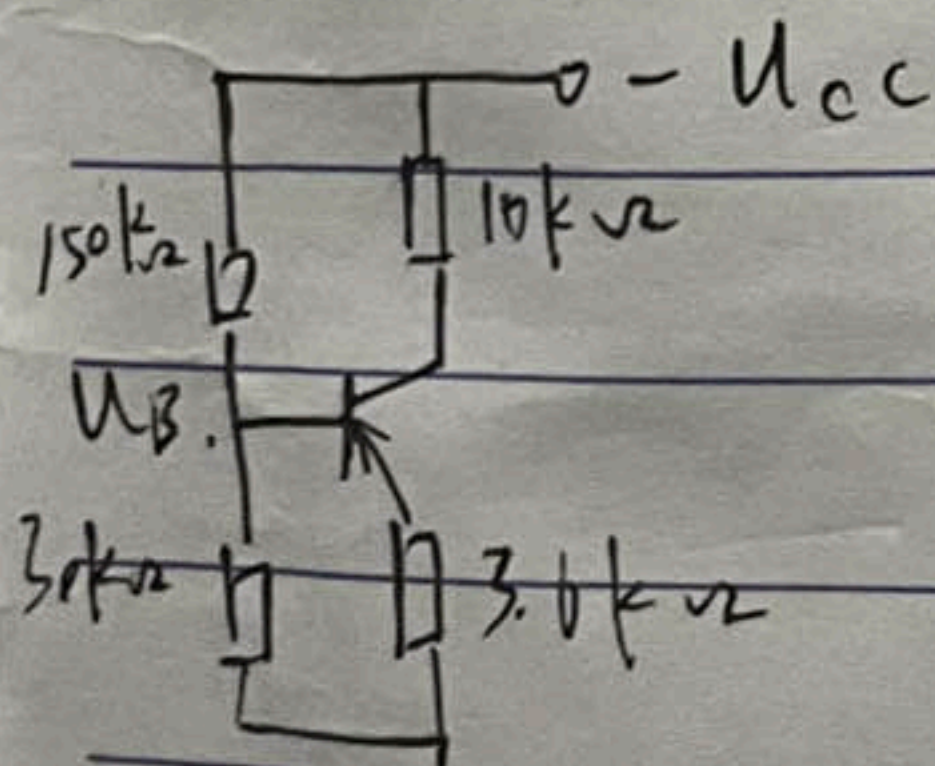

$$U_{B1} = -U_{cc} \times \frac{30k\Omega}{30k\Omega + 150k\Omega} = -2V$$

$$U_{BE1} = -0.7V \Rightarrow I_{E1} = \frac{-0.7V + 2V}{R_E} = 0.56mA$$

$$I_{B1} = \frac{I_{E1}}{\beta+1} = 7.05\mu A, I_C \approx I_E, U_{CE} = -12V + I_C R_C + I_E R_E$$

$$= -1.1V$$

$$\text{又 } U_{BE} = -0.2V$$

$$\text{从而 } U_{E1} = U_{BE} - U_{B1} = -1.8V, I_{E1} = \frac{U_{E1}}{R_E} = 0.5mA$$

$$I_E \approx I_C, I_{B1} = \frac{I_E}{\beta+1} = 9.8\mu A, U_{CE} = -12V + I_{E1}R_E + I_{C1}R_C = -9.2V$$

$$\text{同理有 } U_{B2} = -2V, \text{ 而 } R_{E2} = 1.8k\Omega$$

$$\text{知 } I_{E2} = 1mA \approx I_C, I_{B2} = 19.6\mu A,$$

$$\text{而 } U_{CE2} = -12V + I_{E2}(R_{E2} + R_{C2}) = -4.6V$$

$$\text{而 } U_{CE2} = -12V + (R_{E2} + R_{C2})I_{E2} = -4.6V$$

(2) 由微变等效电路,

$$r_{be1} = r_{bb'} + (1+\beta) \frac{26mV}{I_{E1}} \approx 3k\Omega$$

$$r_{be2} = r_{bb'} + (1+\beta) \frac{26mV}{I_{E2}} \approx 1.6k\Omega$$

$$A_u = A_{u1} \cdot A_{u2} = -\frac{\beta R_{L1}'}{r_{be1}} \cdot \left(-\frac{\beta R_{L2}'}{r_{be2}} \right)$$

$$\text{其中 } R_{L1}' = R_{C1} // 150k\Omega // 30k\Omega // 1.6k\Omega = 1.3k\Omega$$

$$R_{L2}' = 5.6k\Omega // 12k\Omega = 1.5k\Omega$$


$$\text{从而 } A_u = 1016$$

$$(3) r_i = 150k\Omega // 30k\Omega // r_{be1} = 2.68k\Omega$$


$$(4) r_o = 5.6k\Omega$$

6.25

交流通路:

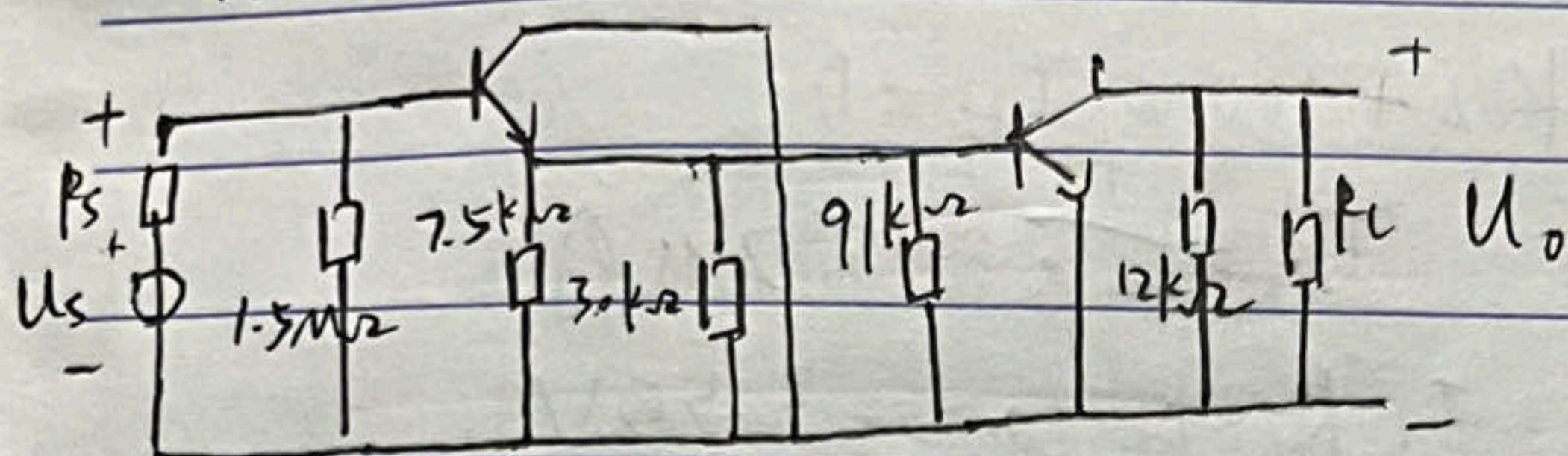

微变等效:

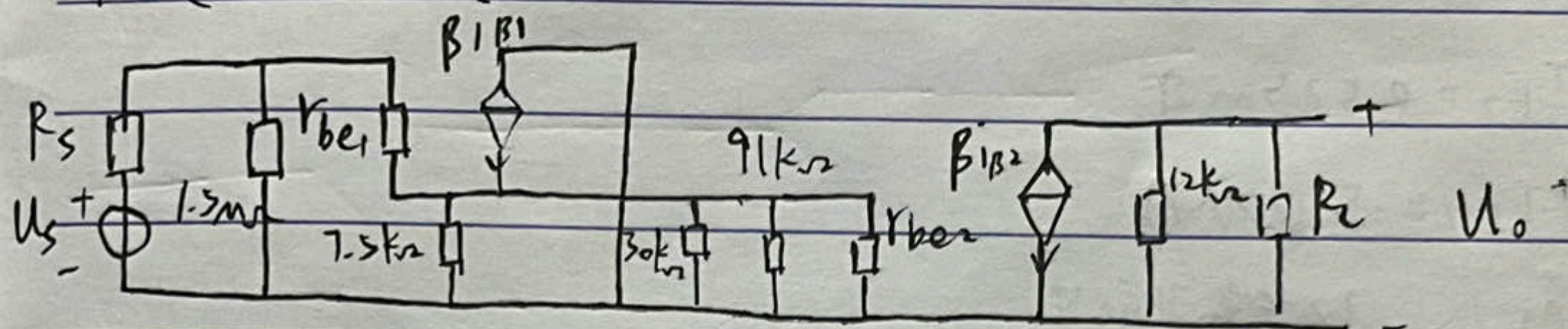

$$(1) R_i = 1.5M\Omega // r_{be1} + (1+\beta)(7.5k\Omega // 30k\Omega // 91k\Omega // r_{be2})$$

$$= 1.5M\Omega // 298.63k\Omega \approx 249k\Omega$$

$$(2) R_o = 12k\Omega$$

$$(3) A_u = A_{u1} \cdot A_{u2}, A_{u1} \approx 1, A_u \approx A_{u2} = \frac{-\beta R_{L2}'}{r_{be2}}$$

$$R_L = \infty \Omega, R_{L2}' = 12k\Omega,$$

$$A_{u2} = -200.$$

$$R_L = 3.6k\Omega, R_{L2}' = 2.8k\Omega$$

$$A_{u2} = -46.7$$

1.28

$$(1) A_u = 100 \Rightarrow \text{电压增益为 } 20\lg|A_u| = 40\text{ dB}$$

$$(2) 20\lg|A_u| = 80\text{ dB} \Rightarrow A_u = 10^4$$

6.37

(1) 直流通路:

$$\text{有 } -6V + U_{BE} + 2I_E \cdot 5k\Omega + 100\Omega \cdot I_E = 0$$

$$\text{得 } I_E = 0.525mA \approx I_C, \quad I_B = \frac{I_E}{1+\beta} \approx 5.2\mu A$$

$$\text{此时有 } U_{CE} = 12V - 2I_E R_E - I_C R_C = 12V - 2 \cdot 0.525mA \cdot 5k\Omega - 0.525mA \cdot 100\Omega = 3.55V$$

$$\text{从而 } U_{CE1} = U_{CE2} = 3.55V$$

$$I_{E1} = I_{E2} = 0.525mA$$

$$I_{B1} = I_{B2} = 5.2\mu A$$

(2) 双端输入, 双端输出

$$A_{ud} = - \frac{\beta(R_C \parallel R_D)}{r_{be}} = -38.8$$

$$r_{id} = 2r_{be} = 30.4\Omega$$

$$(3) A_{uc} = - \frac{\beta R_C}{r_{be} + (1+\beta)(2R_E \parallel r_{be})} = -0.58$$

$$r_{ic} = \frac{1}{2} [r_{be} + (1+\beta) \cdot 2R_E] = 517.78k\Omega$$

$$(4) K_{CMR} = \left| \frac{A_{ud}}{A_{uc}} \right| = 32.9$$