

1.17

$$(1) F = AB + (\bar{A} + B)(C + D + E)$$

$$\bar{F} = (\bar{A} + \bar{B}) \cdot (\bar{A}\bar{B} + \bar{C}\bar{D}\bar{E})$$

$$F' = (A + B)(\bar{A}\bar{B} + CDE)$$

$$(3) F = A \oplus \bar{B} \oplus 1 = \bar{A}\bar{B} + B\bar{A}$$

$$\bar{F} = (\bar{A} + B)(\bar{B} + A) = \bar{A}\bar{B} + \bar{A}B + AB + \bar{B}A = A \odot B = \bar{A} \odot \bar{B}$$

$$F' = (A + \bar{B})(B + \bar{A}) = A \odot B$$

1.18

$$(1) \text{右边} = (AB + BB + AC + BC)(C + A) = [(A+1)B + AC + BC](C + A)$$

$$= \cancel{AB + BB} [(C+1)B + AC] (C + A) = (B + AC)(C + A)$$

$$= AB + ACC + AAC + BC = BC + AB + AC + AC$$

$$= AB + BC + CA = \text{左边}$$

$$(2) \text{左边} = (X\bar{Y} + \bar{X}Y) \oplus Z$$

$$= (X\bar{Y} + \bar{X}Y)\bar{Z} + \overline{X\bar{Y} + \bar{X}Y} \cdot Z$$

$$= X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + (\bar{X} + Y)(X + \bar{Y})Z$$

$$= X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z + X\bar{Y}Z$$

$$\text{右边} = X \oplus (\bar{Y}Z + Y\bar{Z}) = \bar{X}(\bar{Y}Z + Y\bar{Z}) + X\bar{Y}Z + Y\bar{Z}$$

$$= \bar{X}(\bar{Y}Z + \bar{Z}Y) + X(\bar{Y} + \bar{Z})(\bar{Y} + Z)$$

$$= \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}Z + X\bar{Y}\bar{Z} = \text{左边}$$



1.20

$$\begin{aligned} (1) F &= (\overline{A}B + AB\overline{D})(B + CD) = \overline{A}B \cdot \overline{A}B\overline{D} (B + CD) \\ &= (\overline{A} + \overline{B})(\overline{A} + \overline{B} + \overline{D})(B + CD) \\ &= \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D \\ &= \sum m^4(3, 4, 5, 6, 7, 11) \\ &= \prod M^4(0, 1, 2, 8, 9, 10, 12, 13, 14, 15) \end{aligned}$$

$$\begin{aligned} (2) F &= (\overline{A} + C)(A + B)(C + \overline{D}) = (AC + \overline{A}B + BC)(C + \overline{D}) \\ &= \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D \\ &\quad + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D = \sum m^4(4, 6, 7, 10, 11, 14, 15) \\ &= \prod M^4(0, 1, 2, 3, 5, 8, 9, 12, 13) \end{aligned}$$

$$\begin{aligned} (3) F &= (\overline{A} \oplus B)(A \oplus \overline{B}) + B \oplus C \oplus D \\ &= (\overline{A}\overline{B} + AB)(A\overline{B} + \overline{A}B) + (B\overline{C} + \overline{B}C) \oplus D \\ &= AB + \overline{A}\overline{B} + (B\overline{C} + \overline{B}C)\overline{D} + D(B\overline{C} + \overline{B}C) \\ &= \sum m^4(0, 1, 2, 3, 4, 7, 9, 10, 12, 13, 14, 15) \\ &= \prod M^4(5, 6, 8, 11) \end{aligned}$$

1.22

$$(2) F = \sum m^3(2, 6, 7)$$

卡诺图:

|                |                  |    |    |    |
|----------------|------------------|----|----|----|
|                | AB <sub>00</sub> | 01 | 11 | 10 |
| C <sub>0</sub> |                  | 1  | 1  |    |
| 1              |                  |    | 1  |    |

$$\begin{aligned} \text{知 } F &= AB + B\overline{C} \\ &= B(A + \overline{C}) \end{aligned}$$

(3) F =

|                  |                  |    |    |    |
|------------------|------------------|----|----|----|
|                  | AB <sub>00</sub> | 01 | 11 | 10 |
| CD <sub>00</sub> | 0                | 1  | 1  | 1  |
| 01               |                  |    |    |    |
| 11               |                  |    |    |    |
| 10               |                  |    |    |    |

知 F =

(4) F =

|                  |                  |    |    |    |
|------------------|------------------|----|----|----|
|                  | AB <sub>00</sub> | 01 | 11 | 10 |
| CD <sub>00</sub> | 1                | 1  | 1  | 1  |
| 01               |                  |    |    |    |
| 11               |                  |    |    |    |
| 10               |                  |    |    |    |

F =

1.23

(3) F



$$(3) F = \sum m^4(1, 4, 5, 7, 12, 14, 15)$$

|    | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | 0  | 4  | 12 | 8  |
| 01 | 1  | 5  | 13 | 9  |
| 11 | 3  | 7  | 15 | 11 |
| 10 | 2  | 6  | 14 | 10 |

$$\begin{aligned} F &= B\bar{C}\bar{D} + \bar{A}\bar{C}D + BCD + ABC \\ &= (B + \bar{C})(B + C + D)(\bar{A} + C + \bar{D})(A + \bar{C} + D) \end{aligned}$$

$$(4) F = \sum m^4(0, 2, 3, 4, 5, 6, 8, 10, 11, 12, 14) + d(2, 4, 12)$$

|    | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | 0  | 4  | 12 | 8  |
| 01 | 1  | 5  | 13 | 9  |
| 11 | 3  | 7  | 15 | 11 |
| 10 | 2  | 6  | 14 | 10 |

$$\begin{aligned} F &= \bar{D} + \bar{A}B\bar{C} + \bar{B}C \\ &= (B + C + \bar{D})(\bar{B} + \bar{C} + \bar{D})(\bar{A} + C + \bar{D}) \end{aligned}$$

1.23

$$\begin{aligned} (3) F &= \bar{A}\bar{C} + \bar{A}B + \bar{B}\bar{C} = \bar{C}\bar{A} + \bar{C}\bar{B} + B\bar{A} + B\bar{B} \\ &= \bar{C}(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) = \bar{C}\overline{AB} + B\overline{AB} \end{aligned}$$



象问题及其解


逻辑电路, 简称  
输入信号, 而  
输入信号, 而  
用十分广泛。  
然后介绍组合  
象问题及其

再将其划分  
的规划设计  
与设计相反  
进行技术交  
结构化设计  
这些文档要

同的主要信  
系统的轴  
个简单计

$$= \overline{\overline{C} \overline{AB}} \cdot \overline{\overline{B} \overline{AB}}$$

电路图:

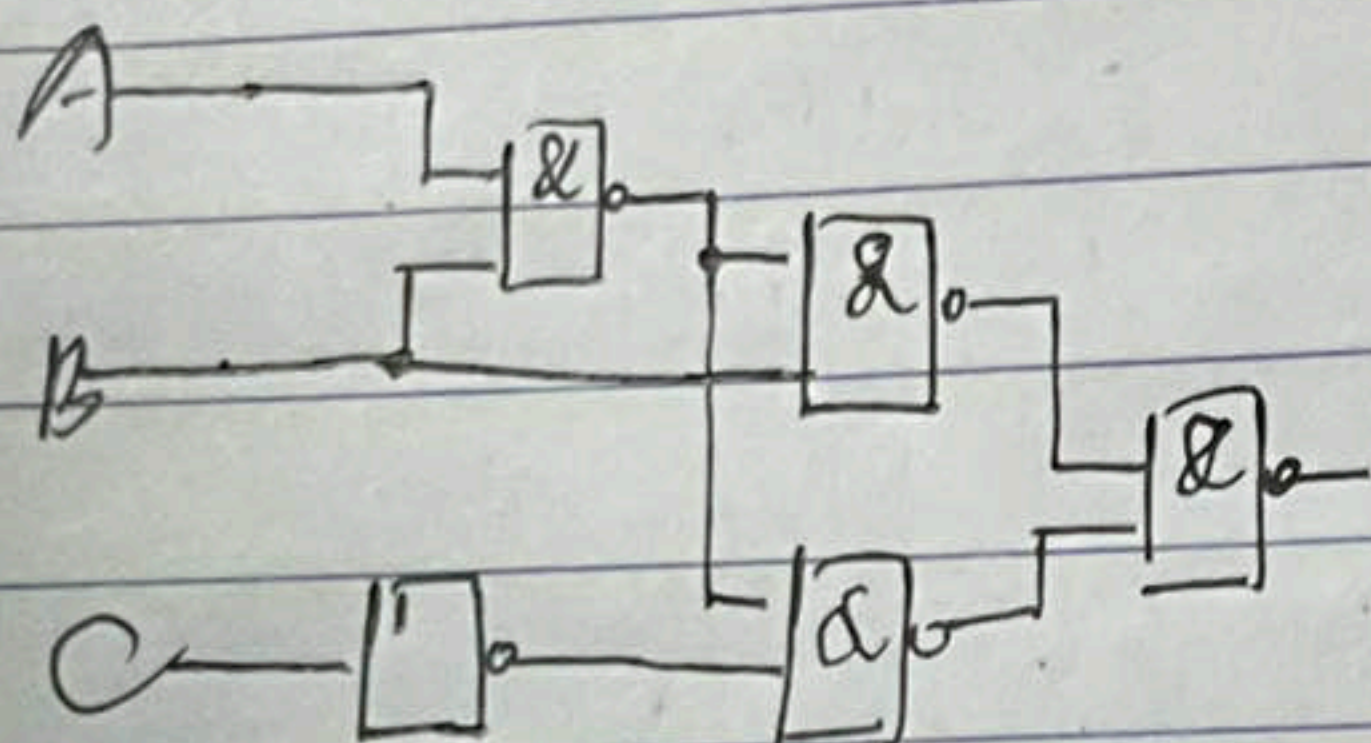


$$(4) F = (\overline{A} + \overline{B})(AB + C)$$

$$= \overline{A}C + \overline{B}C$$

$$= C(\overline{A} + \overline{B}) = \overline{\overline{A}C \cdot \overline{B}C}$$

电路图:

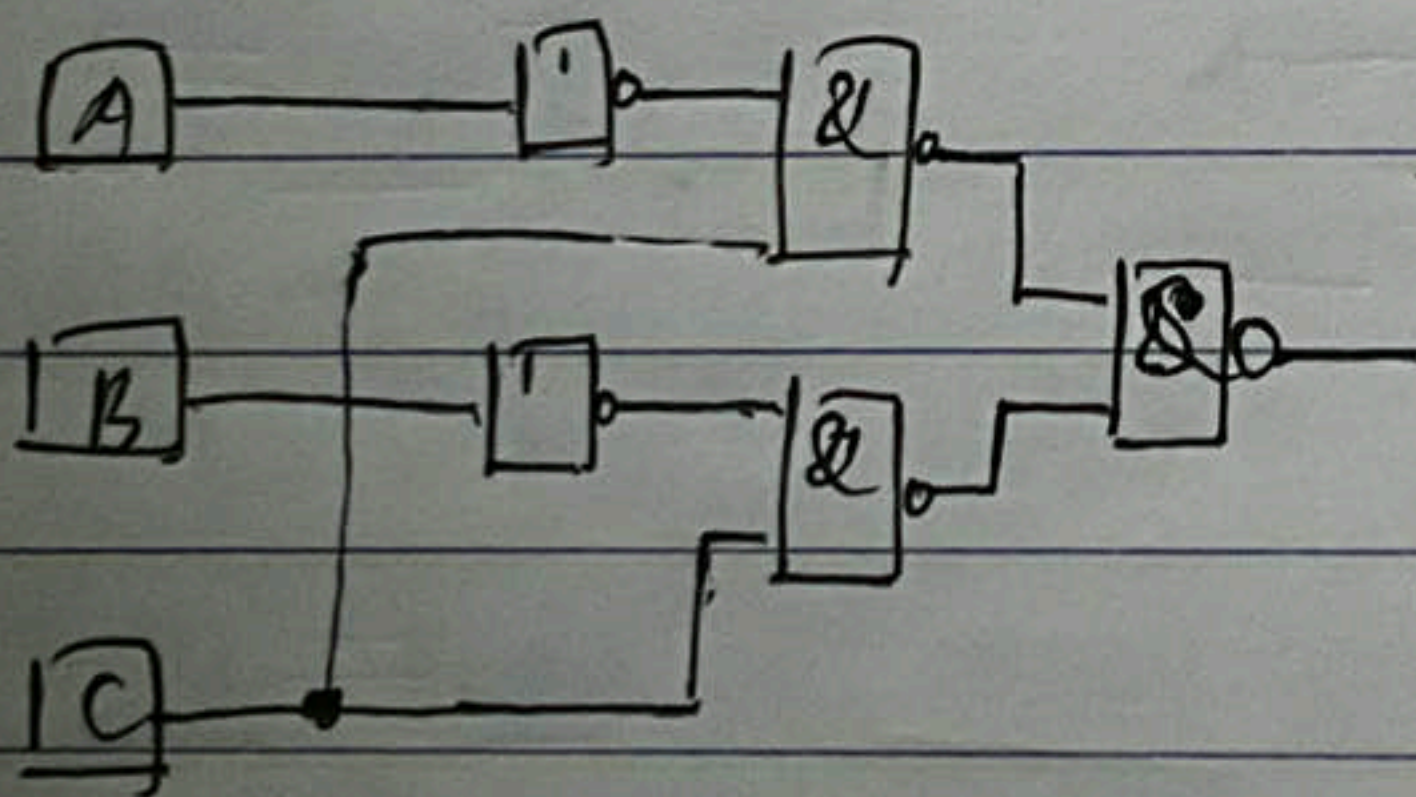

1.24

| AB   | 00 | 01 | 11 | 10 |
|------|----|----|----|----|
| C=00 |    |    | 1  |    |
| 01   |    |    | 1  |    |
| 11   |    | 1  |    |    |
| 10   |    | 1  |    |    |

$$F = \overline{A}BC + A\overline{B}C$$

$$= B(A \oplus C)$$

$$= AB \oplus BC$$

$$\text{故 } W=A, X=B, Y=B, Z=C$$

1.25

前 2 位用

后 4 位用

00 黑木


01 红木

10 梅


11 方

1.26

(1)

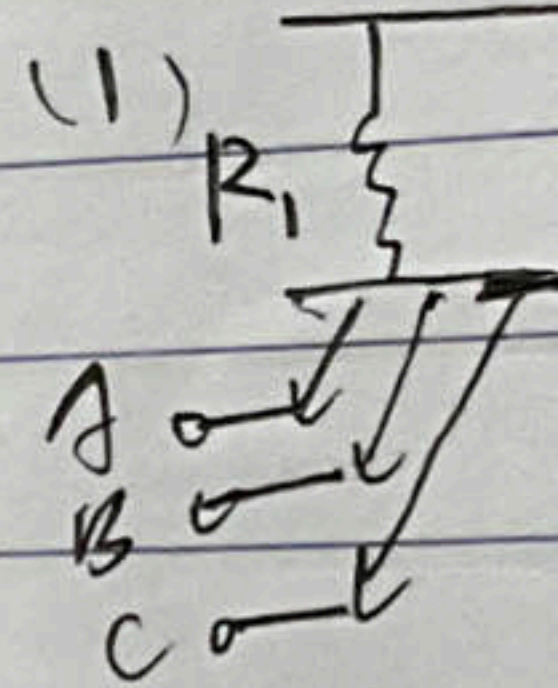

(3)

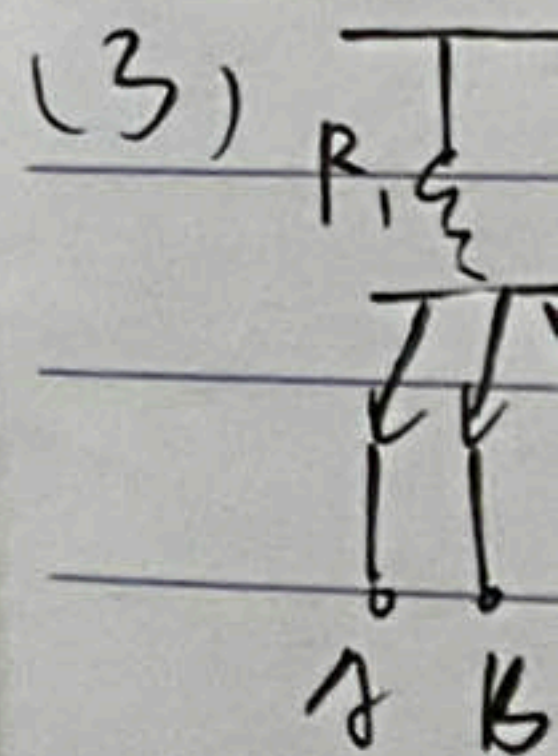





1.25

前2位用二进制表示花色

后4位用以表示数字

|       |        |         |        |
|-------|--------|---------|--------|
| 00 黑桃 | A 0001 | 7 0111  | K 1101 |
| 01 红心 | 2 0010 | 8 1000  |        |
| 10 梅花 | 3 0011 | 9 1001  |        |
| 11 方块 | 4 0100 | 10 1010 |        |
|       | 5 0101 | 11 1011 |        |
|       | 6 0110 | 12 1100 |        |

1.26

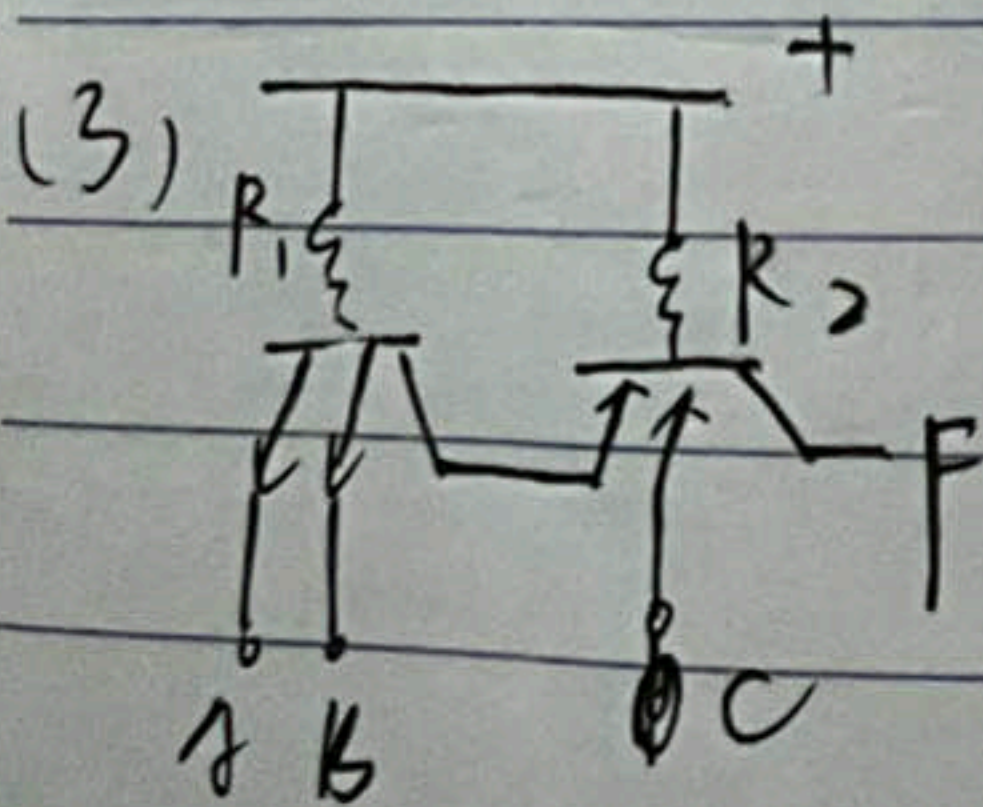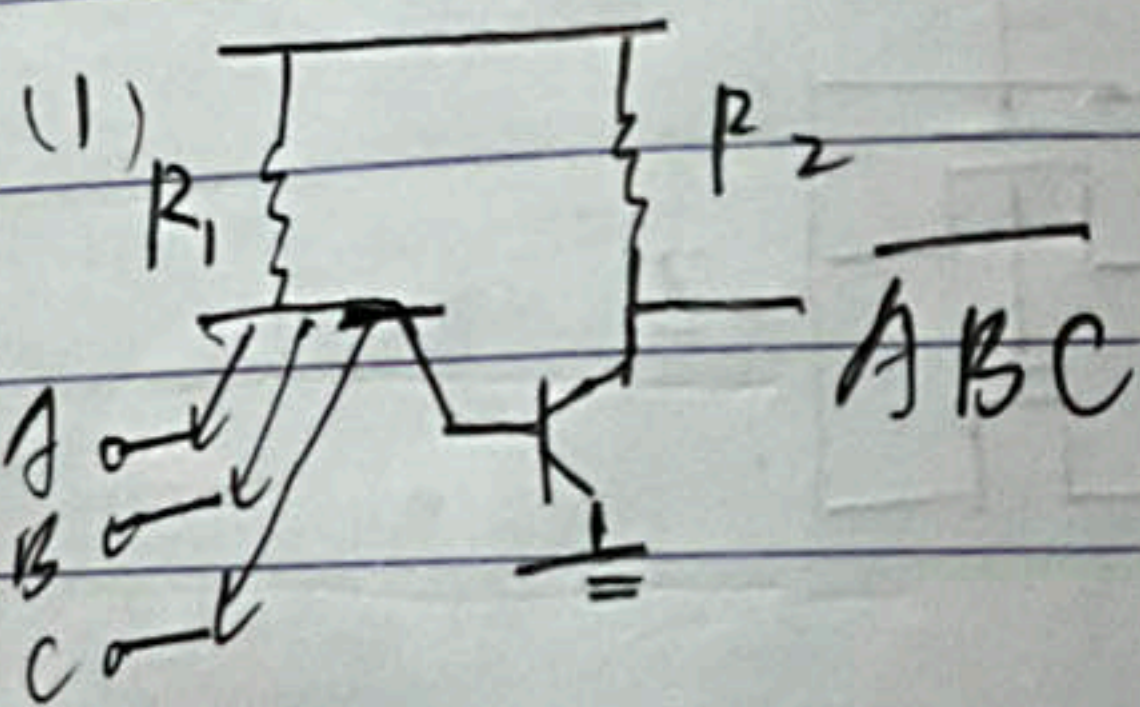



1.28

有极性输出指前出调整为上拉支路 $Q_4$ 管和下拉支路 $Q_3$ 管构成集电极开路门指前如同TTL门一样形成线与结构  
三态门优点: 实现线与、有效减小负载效应、功耗。

1.29


CMOS由PMOS、NMOS组成。用互补信号控制

PMOS传送"1"良好, NMOS传送"0"良好


control = 1, 二者均导通, "1" "0"可传送

0, 二者均不导通, 不传送"1" "0"


非门:

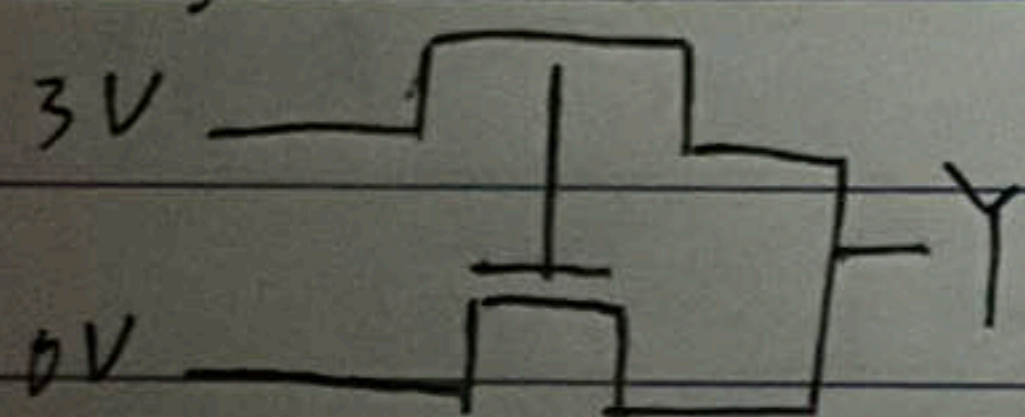

与非门:

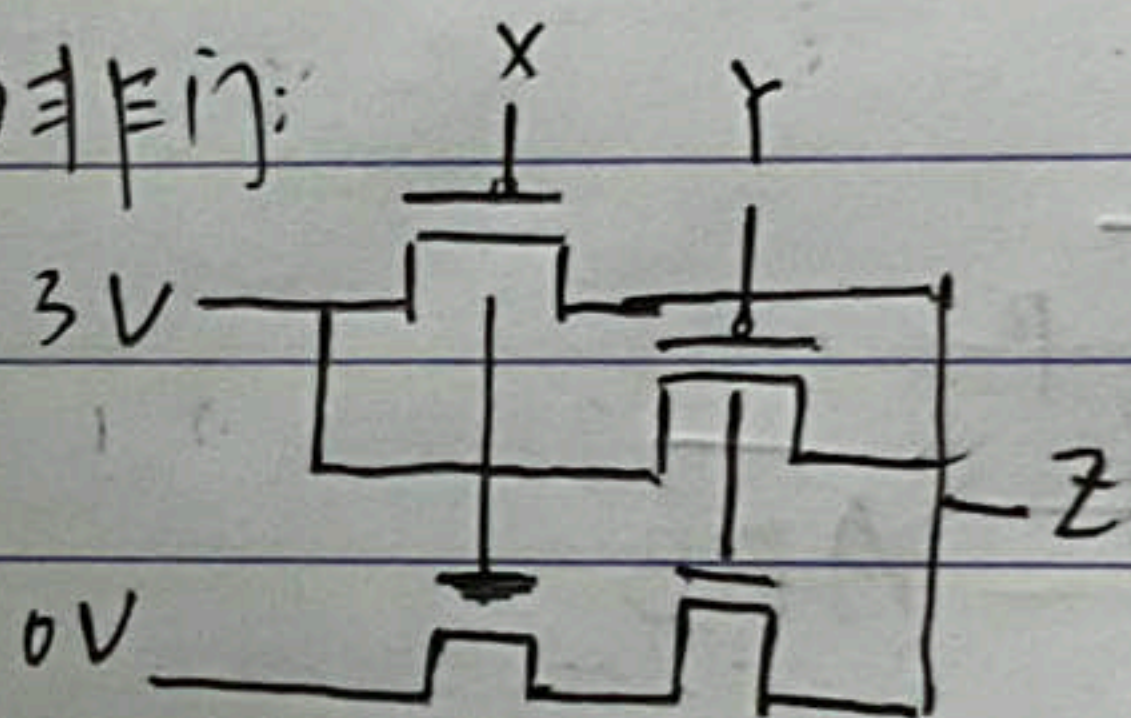

或非门:

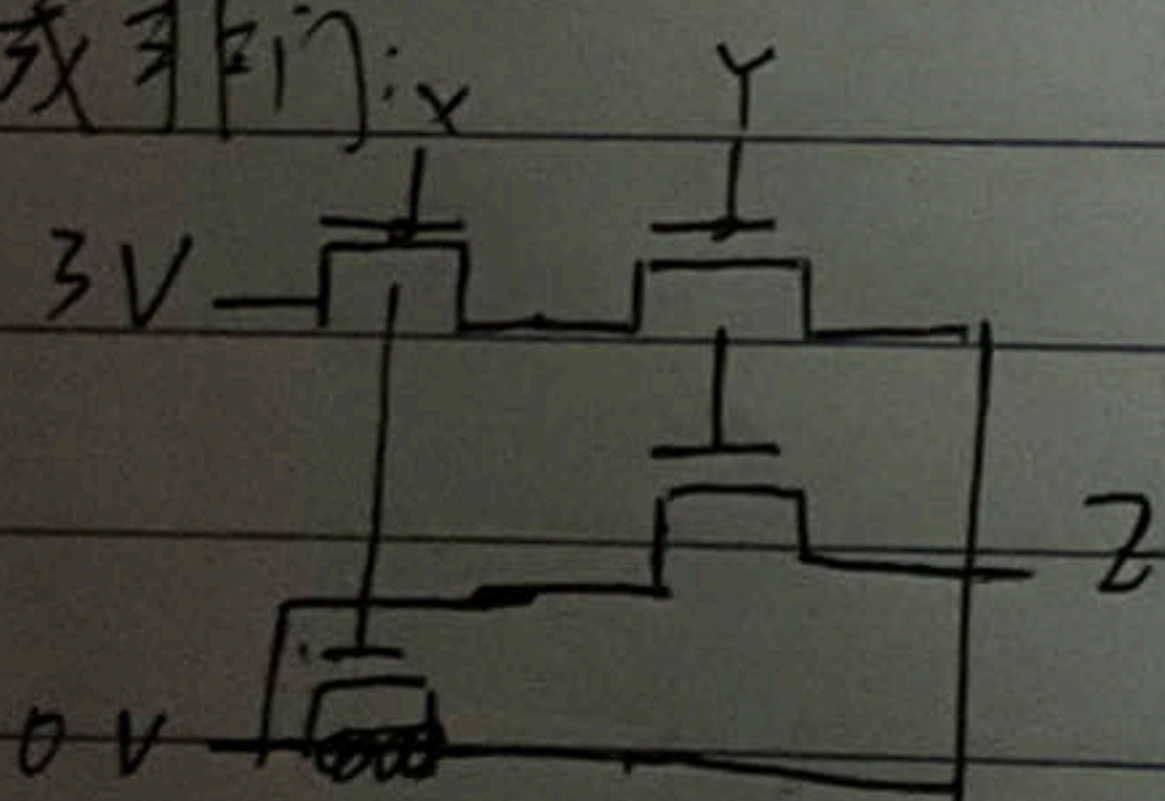

1.30

工艺: CMOS电路, TTL电路 2类

规模: 小规模集成电路, 中规模集成电路, 大规模集成电路

超大规模

特性: 负载

1.11) 10

降算法:

10000

除法: 1

2500 / 2

625 / 2

156 / 2 =

39 / 2 =

9 / 2 =

2 / 2 =

逆序有





超大规模集成电路、超大规模集成电路

特性：负载能力、延迟特性、功耗特性、引脚处理